


Current in circuits

1. The two lamps in the circuit are identical.

$$I_1 = 0.5\text{A}, I_2 = 0.2\text{A}$$

- (a) What are the currents:

- (i) I_3 ,
- (ii) I_4 ,
- (iii) I_5 ?

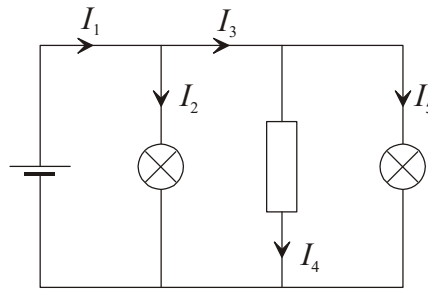

- (b) How much charge passes through the battery in one second?


2. In this circuit, $I_1 = 0.25\text{A}$, $I_2 = 0.15\text{A}$

- (a) What are the currents:

- (i) I_3 ,
- (ii) I_4 ?


- (b) How much charge passes through the resistor in one minute?

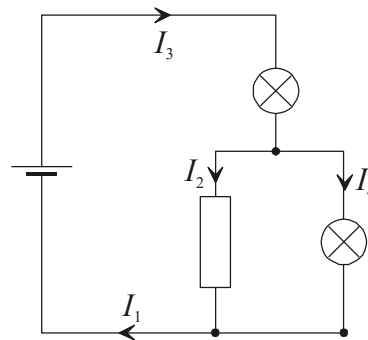- (c) What would be the current I_3 if the filament in the top lamp broke?



3. In this circuit the three lamps, A, B & C, are identical. S is a switch. Compare the brightness of lamps A, B & C (e.g. equal, brighter, dimmer, off):

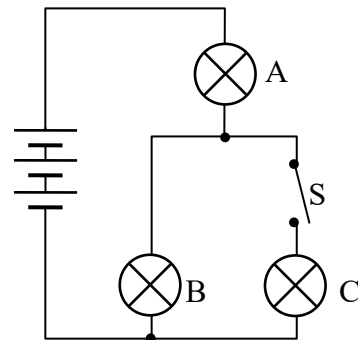- (a) with S open (off),
- (b) with S closed.



4. Draw a diagram of a circuit using two switches, a battery and a lamp, so that the bulb will light:

- (a) only if *both* switches are pressed,
- (b) if *either* switch is pressed (or both).

(1: 0.3A , 0.1A , 0.2A , 0.5C . 2: 0.25A , 0.1A , 9C , 0A .)