
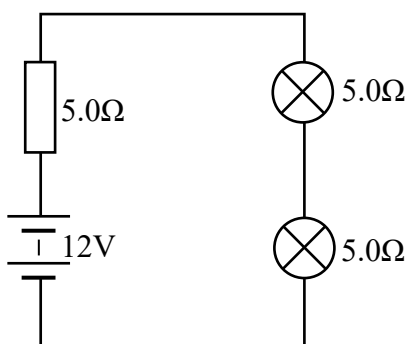


Further electrical circuit questions

1. In the following circuits the lamps are identical.

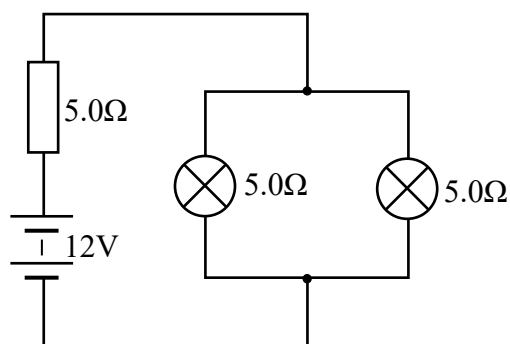

circuit 1




circuit 2

- (a) For circuit 1, calculate:
- (i) the current flowing through each lamp,
 - (ii) the power dissipated in each lamp.
- (b) For circuit 2, calculate the current flowing through each lamp.
- (c) (i) Explain how the brightness of the lamps in circuit 1 compares with the brightness of the lamps in circuit 2.
 (ii) Explain why the battery would last longer in circuit 1.
- (d) One of the lamps in circuit 2 breaks and no longer conducts. Describe and explain what happens to the brightness of the other lamps.


(0.8A, 3.2W; 0.8A; same, less current; brighter)

2. Two identical resistors can be connected to a power supply in two ways, circuit A, or circuit B.

 - (i) In which circuit is the total power larger?
- (ii) How many times larger is it?




circuit A

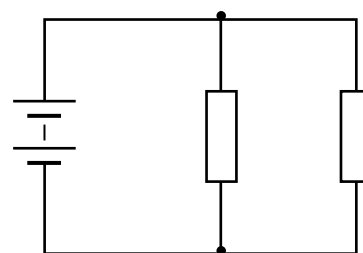


circuit B

(B, 4x)

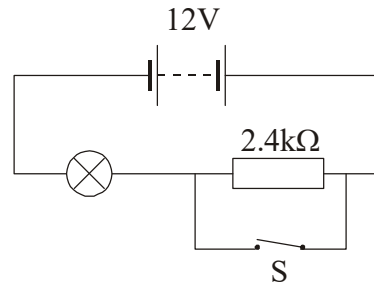3. (a) Calculate the current in a 12V, 36W lamp when it is connected to a 12V supply:
- directly, (3.0A)
 - in series with a 2.4k Ω resistor. ($5.0 \times 10^{-3}A$)
- (b) When the 2.4k Ω resistor is suddenly put into the circuit by opening switch S, the voltage across the lamp takes a few seconds to fall to its final value. Explain why this is so.



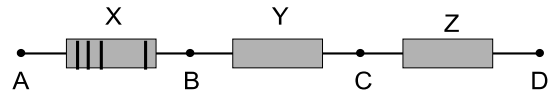4. Three unknown components, X, Y and Z, are connected in series. Component X is a resistor, with bands: brown, black, orange, silver.




A battery is connected between A and D, first one way round, then the other. The table shows the results of connecting a voltmeter between AB, BC and CD.


	one way	other way
AB	2.6V	0V
BC	0.6V	-9V
CD	5.8V	0V

Identify X, Y and Z as fully as you can. (*ans @ end)

5.

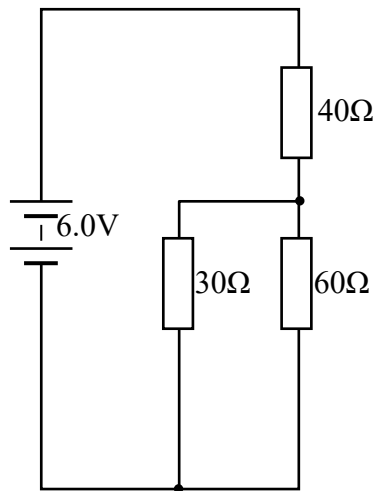

(a)

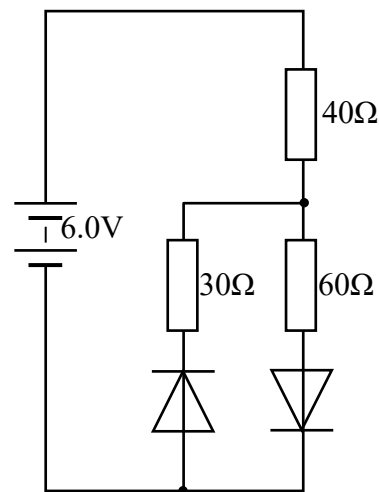

(b)

- (a) For the circuit (a), calculate:
- the current in the 30 Ω resistor,
 - the current in the 60 Ω resistor,
 - the voltage across the 40 Ω resistor
- (b) For the circuit (b), calculate:
- the current in the 30 Ω resistor,
 - the current in the 60 Ω resistor,
 - the voltage across the 40 Ω resistor


(67mA, 33mA, 4.0V; 0A, 54mA, 2.16V)

6. In this circuit, each resistor has a resistance of 100Ω .


The battery voltage is $12V$.

- (a) Calculate the voltage between C and F.
- (b) When a resistor R is connected between D and F, there is zero voltage between C and F.
 - (i) Calculate the value of resistor R.
 - (ii) Calculate the current that flows from the battery in this case.


($4V$; 67Ω , $0.12A$)

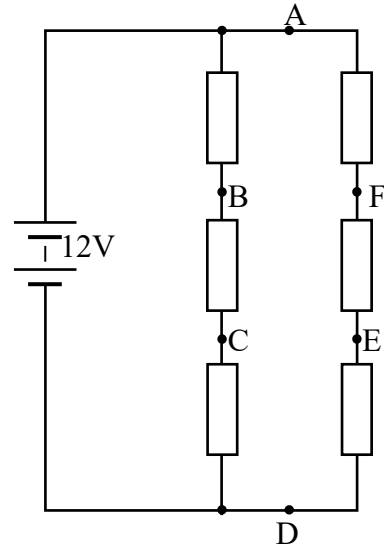

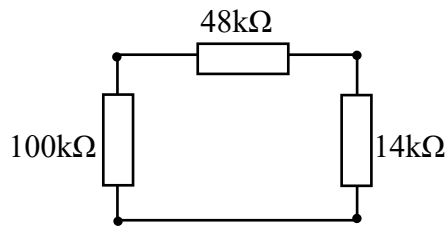7. This question is about detecting possible faults in the soldered joints of this circuit.




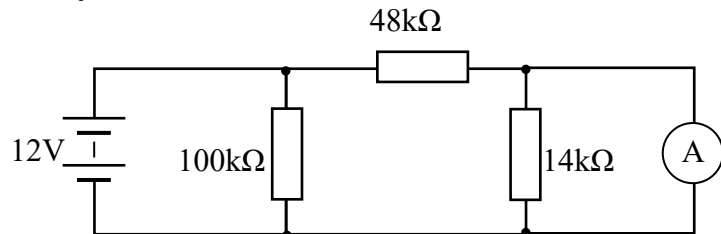- (a) In the first test, a $12V$ supply and an ammeter were connected, as shown. Calculate the expected current in the ammeter.



- (b) The ammeter was then replaced by a voltmeter, which gave a reading of $2.7V$. Show that this is the reading you would expect.

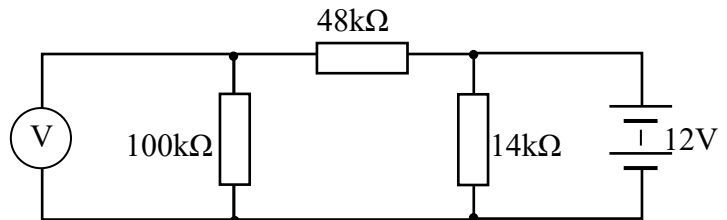- (c) In the final test, the $12V$ supply and the voltmeter were connected as shown. This time, the voltmeter reading was almost $12V$, showing a fault in the circuit connections. What was the fault?



($0.25mA$, $100k\Omega$ not connected)

*($Qu4: 10k\Omega$, diode, $22k\Omega$)