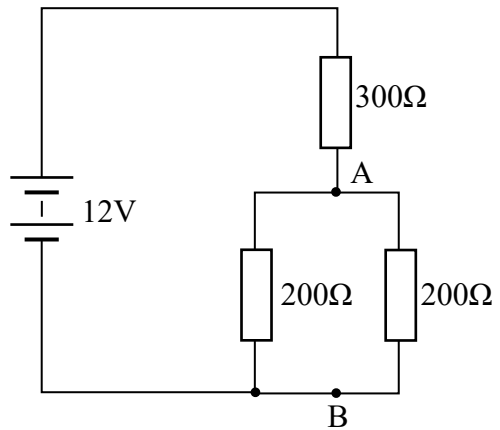


Potential Dividers

1. Three resistors are connected to a 12V battery as shown.

- (a) What is the equivalent resistance of the two 200Ω resistors in parallel?
 (b) What is the voltage between A and B?
 (c) What is the voltage across the 300Ω resistor?


(100Ω, 3V, 9V)



2. The voltmeter in this circuit reads 6.2V.

- (a) What is the voltage across the 10kΩ resistor?
 (b) What is the resistance of the resistor R?

(2.8V, 22kΩ)

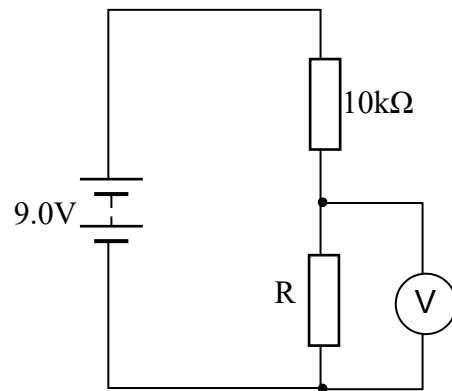


3. In this circuit, what is the ratio of:

(a) $\frac{I_1}{I_2}$

(b) $\frac{V_1}{V_2}$


(2, 2)

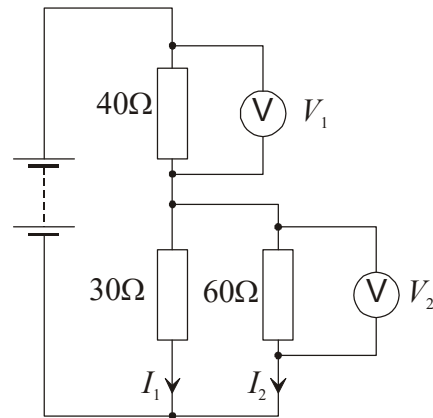

- 4.

- (a) What is the voltage between A & C?
 (b) What is the voltage between B & D?
 (c) What would a voltmeter read if connected between A & B?


(8V, 6V, 2V)

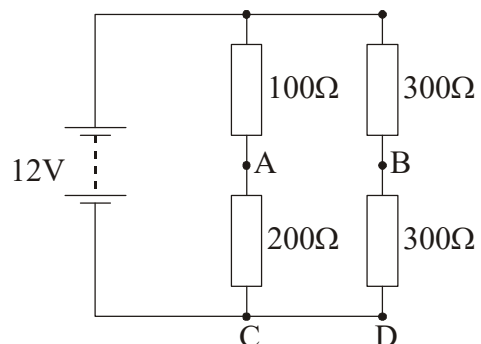

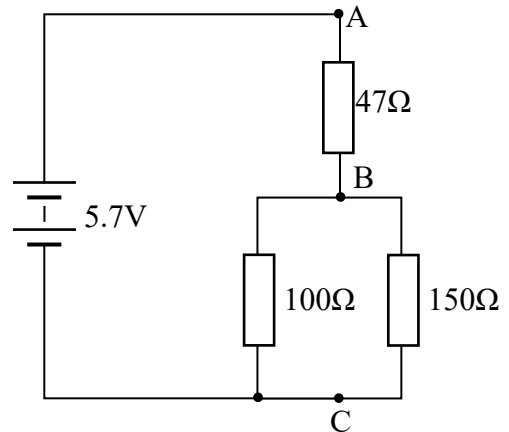5. Three resistors, of resistance 47Ω , 100Ω and 150Ω are connected to a battery as shown. A voltmeter connected across the battery reads $5.7V$.

Calculate


- the resistance of the circuit between B and C. (60Ω)
- the voltage between A & B and between B & C. ($2.5V$, $3.2V$)
- the current through the 47Ω resistor, the 100Ω resistor and the 150Ω resistor. ($53mA$, $32mA$, $21mA$)



6. A series circuit is connected as shown in the diagram.

- What is the potential difference between A and B?
- An additional resistor of 100Ω is connected between the 50Ω resistor and the cells. What is the voltage between A and B now?
- The additional 100Ω resistor is now connected in parallel with the first 100Ω resistor. What is the voltage between A and B now?

($4V$, $2.4V$, $3V$)

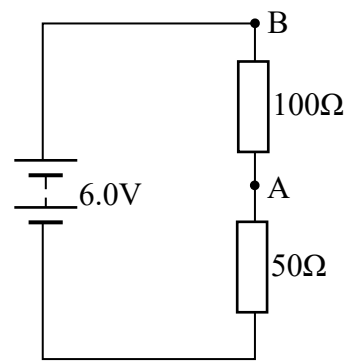



7. The resistance of a light dependent resistor (LDR) decreases as the light intensity increases.

An LDR is connected in series with a $6.0k\Omega$ resistor as part of a light level sensor circuit.

- What is the output voltage V , when the resistance of the LDR is
 - $6.0k\Omega$ (in the dark)
 - $3.0k\Omega$
 - $2.0k\Omega$ (in the light)

($4.5V$, $3.0V$, $2.25V$)

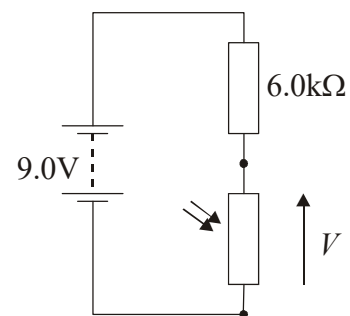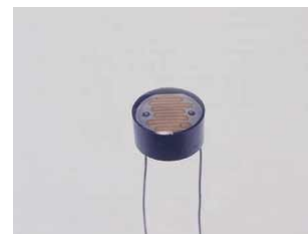- How would you alter the circuit so that the output V increases with increasing light level?



8. A catalogue states that, when a particular light emitting diode (LED) is used with a 5V supply, a 270Ω resistor must be connected in series to limit the current to 10mA.

Calculate:



- (i) the voltage across the resistor,
- (ii) the voltage across the LED,
- (iii) the resistance of the LED in these conditions.

(2.7V, 2.3V, 230Ω)

9. The resistance of a **thermistor** changes with temperature. The graph shows the characteristic of a thermistor.

(Note that the resistance scale is not linear – it is **logarithmic**.)

thermistor characteristic curve

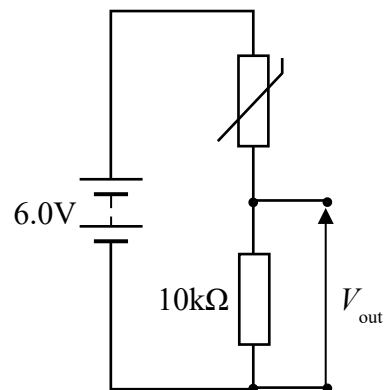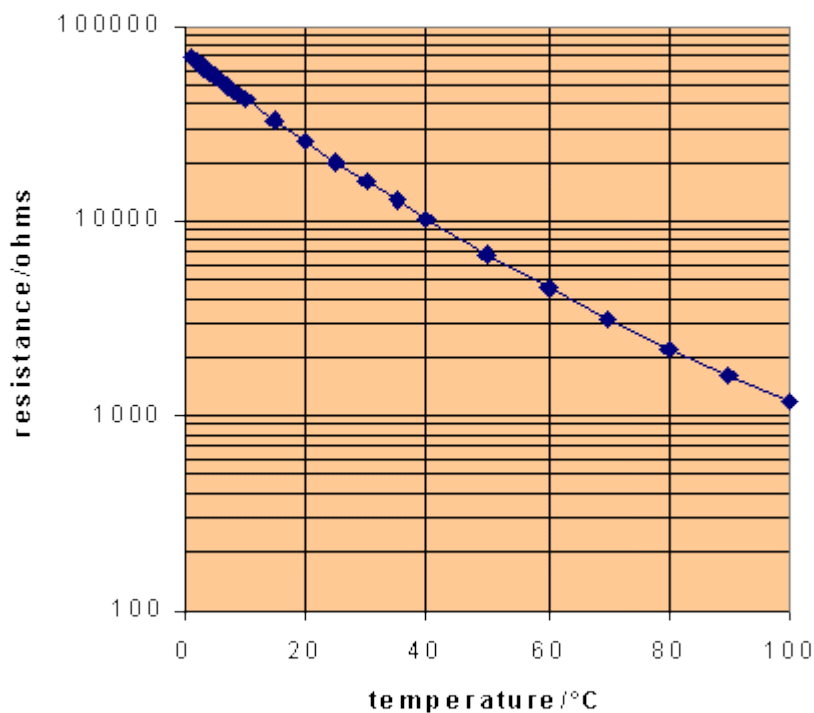

This thermistor is used with a $10\text{k}\Omega$ resistor in a temperature sensor, in the circuit shown.

Calculate the output voltage V_{out} at:

- (i) 40°C ,
- (ii) 80°C .

(3.0V, 5.9V)