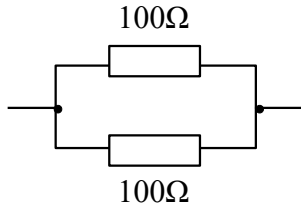


# Resistors in series and parallel


---

1. Without detailed calculation, state the resistance of each of these combinations of resistors.

(a)




(b)

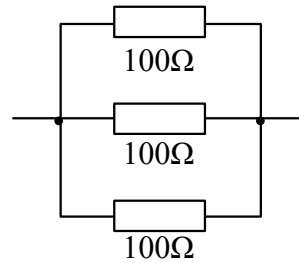


2. What is the resultant resistance of each of the following combinations of resistors? ( $120\Omega$ ,  $400\Omega$ ,  $55\Omega$ ,  $100\Omega$ ,  $167\Omega$ ,  $133\Omega$ )


(a)

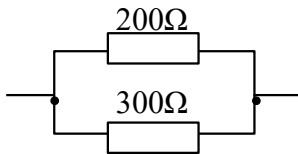


(b)

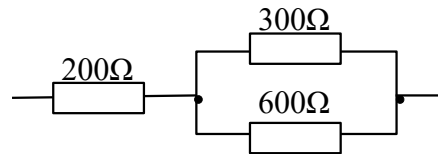


(c)

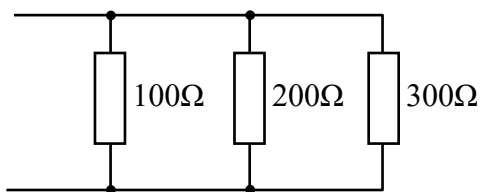


(d)

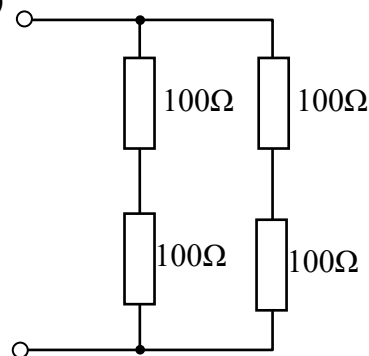

(e)

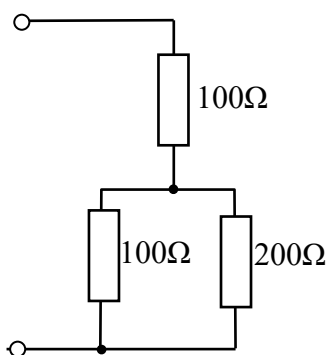

(f)

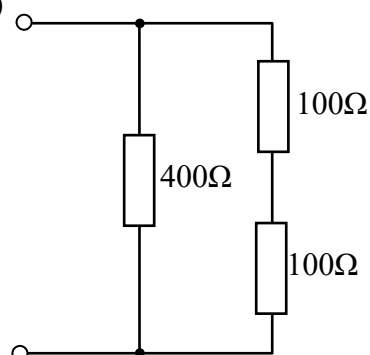


3. Resistors of  $100\Omega$  and  $150\Omega$  are joined, first in series, then in parallel.

What is the total resistance:

- (i) in series? ( $250\Omega$ )
- (ii) in parallel? ( $60\Omega$ )

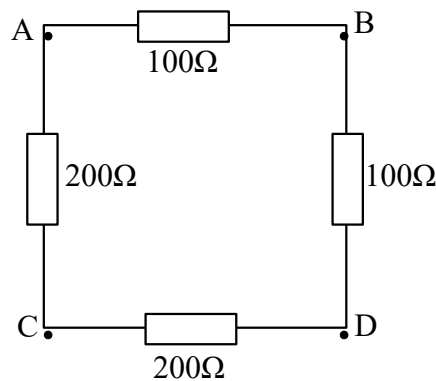4. A connecting lead used in a laboratory consists of 55 strands of wire, each of resistance  $2.3\Omega$ . What is the resistance of the wire? ( $0.042\Omega$ )
5. What is the total resistance when:
- two  $1\text{k}\Omega$  resistors are connected in parallel? ( $500\Omega$ )
  - ten  $1\text{k}\Omega$  resistors are connected in parallel? ( $100\Omega$ )
6. Four resistors, two  $100\Omega$  and two  $200\Omega$ , are arranged in a square as shown.



What resistance would be measured between the points:

- AB? ( $83\Omega$ )
  - AC? ( $133\Omega$ )
  - AD? ( $133\Omega$ )
7. You are given one  $200\Omega$  resistor and two  $100\Omega$  resistors. Draw diagrams to show how you would connect any combination of them to give a combined resistance of:
- $400\Omega$ ,
  - $250\Omega$ ,
  - $167\Omega$ .
8. Resistors are manufactured only in certain values. In the laboratory there are resistors with the values  $1\text{k}\Omega$ ,  $2.2\text{k}\Omega$ ,  $3.3\text{k}\Omega$ ,  $4.7\text{k}\Omega$ ,  $5.6\text{k}\Omega$  and  $6.8\text{k}\Omega$ . How can you combine two or more of these resistors when you need a resistance of:
- $3.0\text{k}\Omega$ ,
  - $9.0\text{k}\Omega$ ,
  - $500\Omega$ ,
  - $5.0\text{k}\Omega$ ,
  - $4.0\text{k}\Omega$ ?
9. (a) What is the smallest number of resistors you need to make a resistance of:
- $5\Omega$ , given a supply of  $3\Omega$  resistors? ( $4$ )
  - $7\Omega$ , given a supply of  $4\Omega$  resistors? ( $5$ )
- (b) Draw a diagram, in each case, to show how you would connect them.